

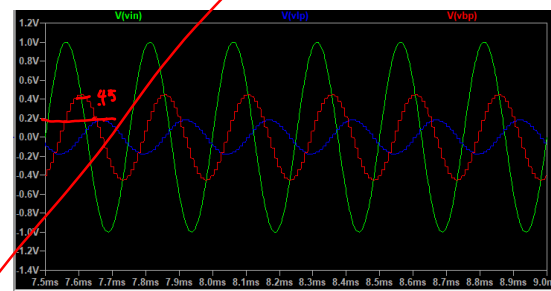
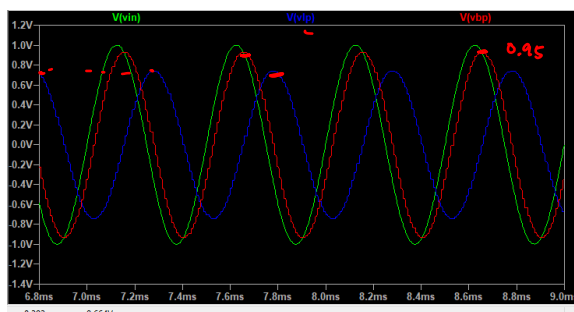
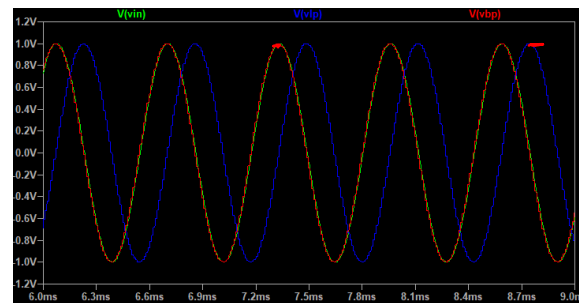
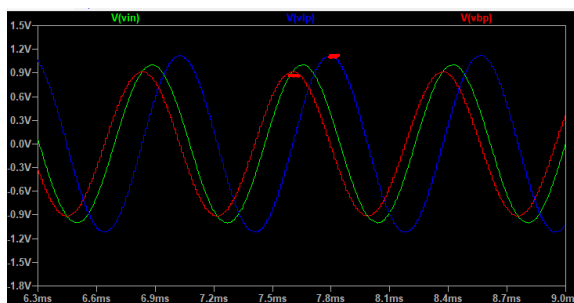
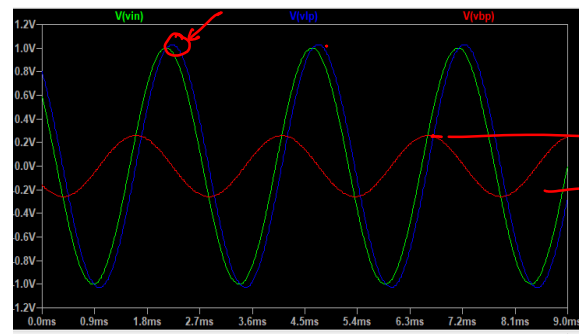
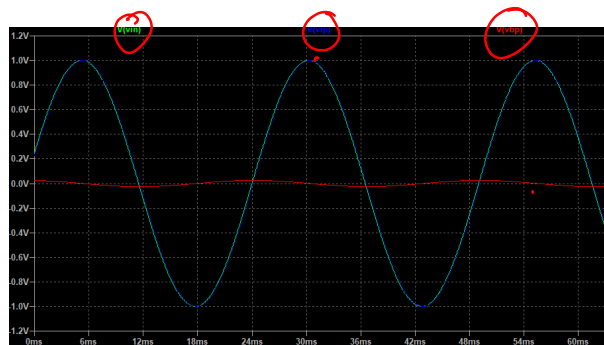


Lecture 18 - Signal Generators 2


Wednesday, October 25, 2023 5:38 PM

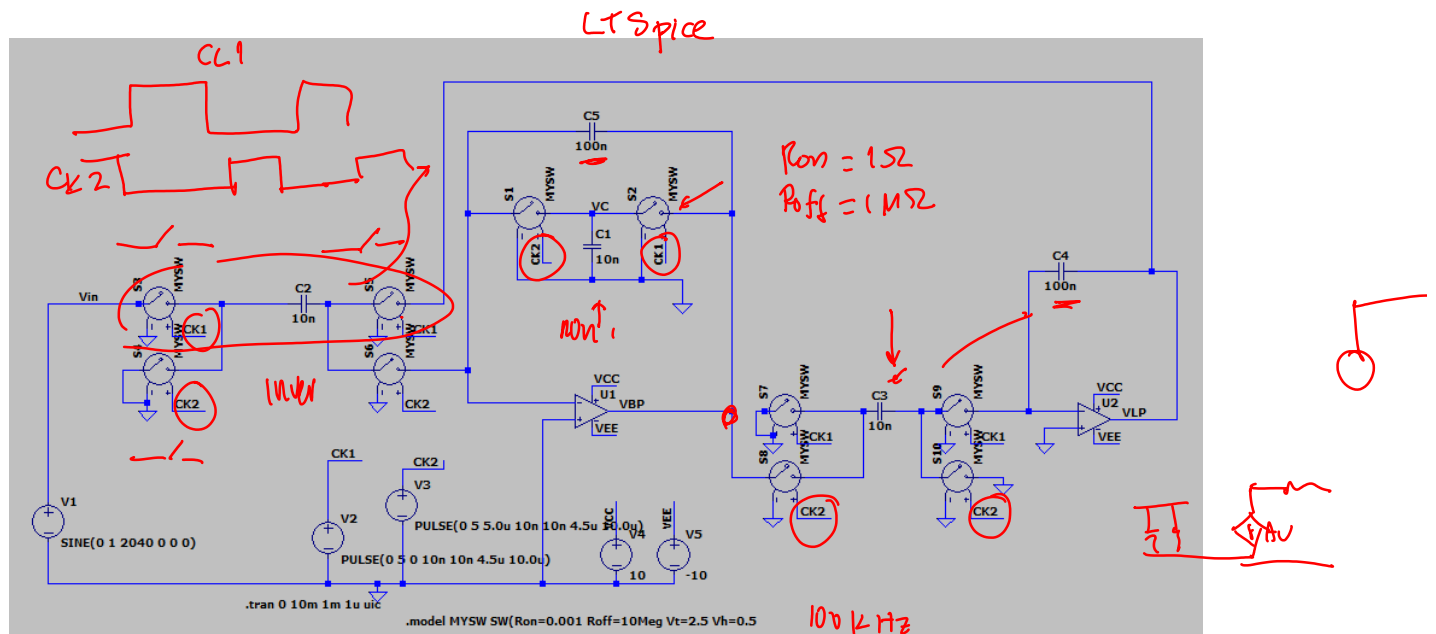

ZINIZ

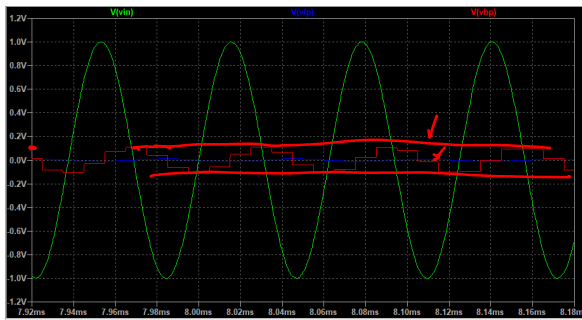

16KHz

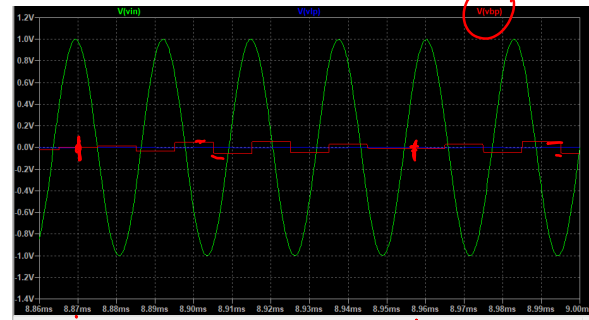


44KHz

50

100 KHz



Wien-Bridge Oscillator

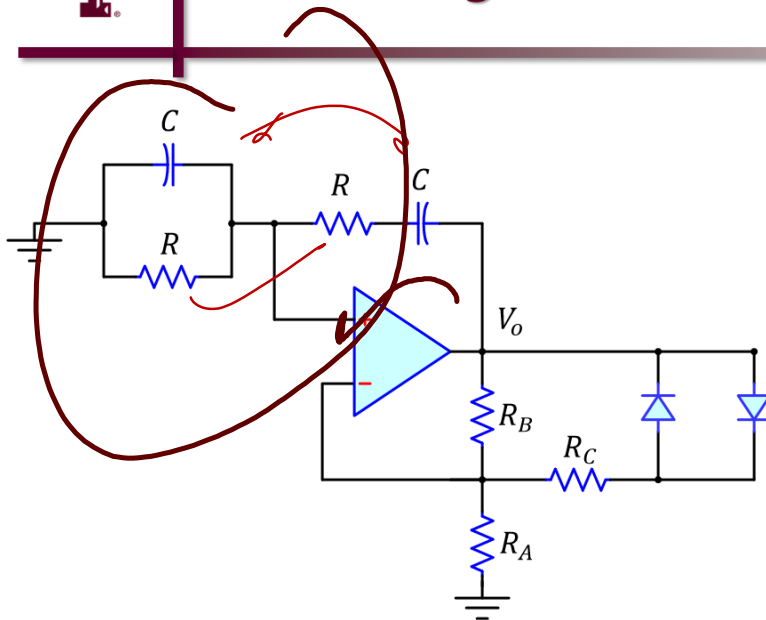For $T(j\omega_0) > 1$,

$$A = \frac{V_o}{V_p} = 1 + \frac{R_B}{R_A}$$

$$V_p = \frac{Z_p}{Z_p + Z_s} V_o = \frac{\frac{R}{1 + sRC}}{\frac{R}{1 + sRC} + \frac{1 + sRC}{sC}} =$$

$$B(j\omega) = \frac{V_p}{V_o} = \frac{s/\omega_o}{s^2 + 3\frac{s}{\omega_o} + \omega_o^2}, \text{ where}$$


$$T(j\omega) = \frac{1 + \frac{R_B}{R_A}}{s^2 + 3\frac{s}{\omega_o} + \omega_o^2}$$

At resonant frequency $|T(j\omega_0)|$ Therefore, for sustained oscillations, $\frac{R_B}{R_A} \geq 3$

© Oscar Moreira



Wien-Bridge Oscillator

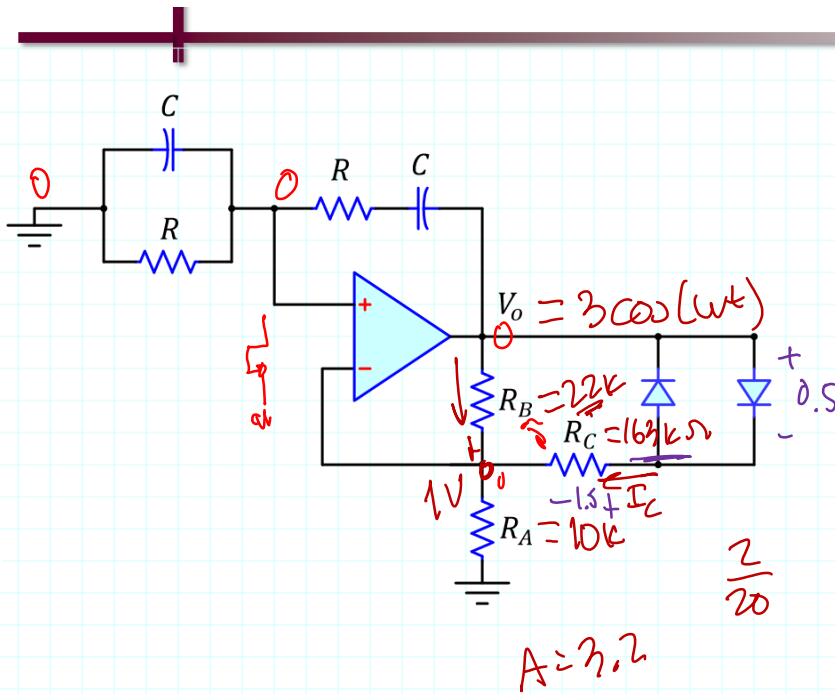



Design an oscillator such that it produces $V_o = 3 \cos(\omega t)$, and $\omega = 1 \text{ KHz}$

- For sustained oscillations, $\frac{R_B}{R_A} > 2$
- Example:
- Let $R_B = 22k\Omega$ and $R_A = 10k\Omega$, $\left(\frac{R_B}{R_A} = 2.2\right)$
- At the peak value we want to reduce the amplitude, therefore:
- $I_B = \frac{2V}{22k\Omega}$, must fall to $I_B = \frac{2V}{20k\Omega}$ (circuit is added)
- $I_C = \frac{2V}{22k\Omega} - \frac{2V}{20k\Omega} = 9.09 \mu A$
- Use diode equation with $I_0 = 1 \times 10^{-15} \text{ A}$
- $I_D = I_0 e^{\frac{V_D}{V_T}} \Rightarrow V_D = V_T \ln\left(\frac{9.09 \mu A}{I_0}\right)$
- $R_C = \frac{2 - 0.515}{9.091 \mu A} = 163k\Omega$

© Oscar More.

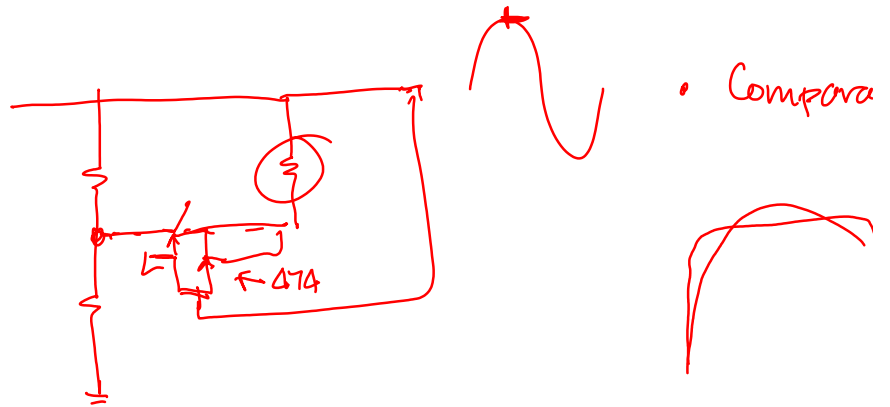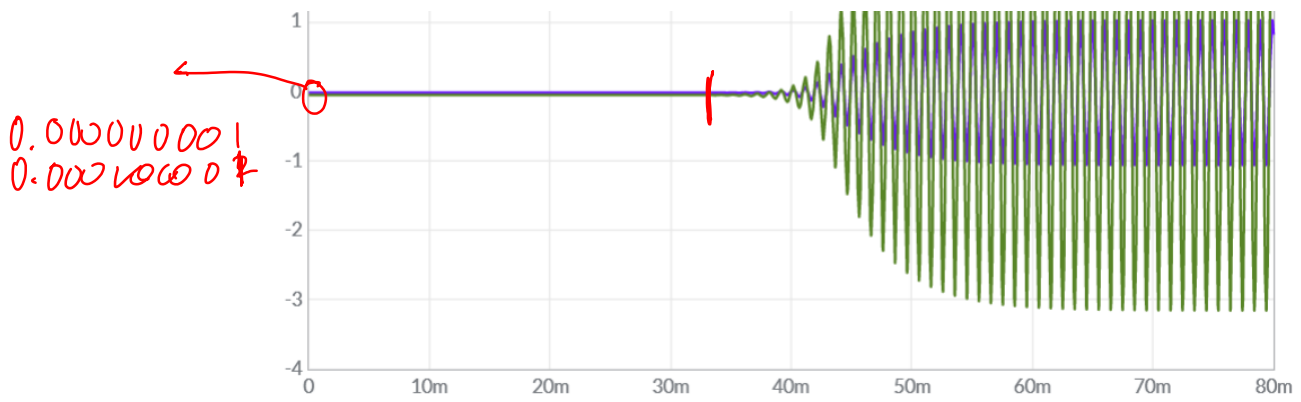
Make sure V_T is determined according to the simulation temperature





Wien-Bridge Oscillator

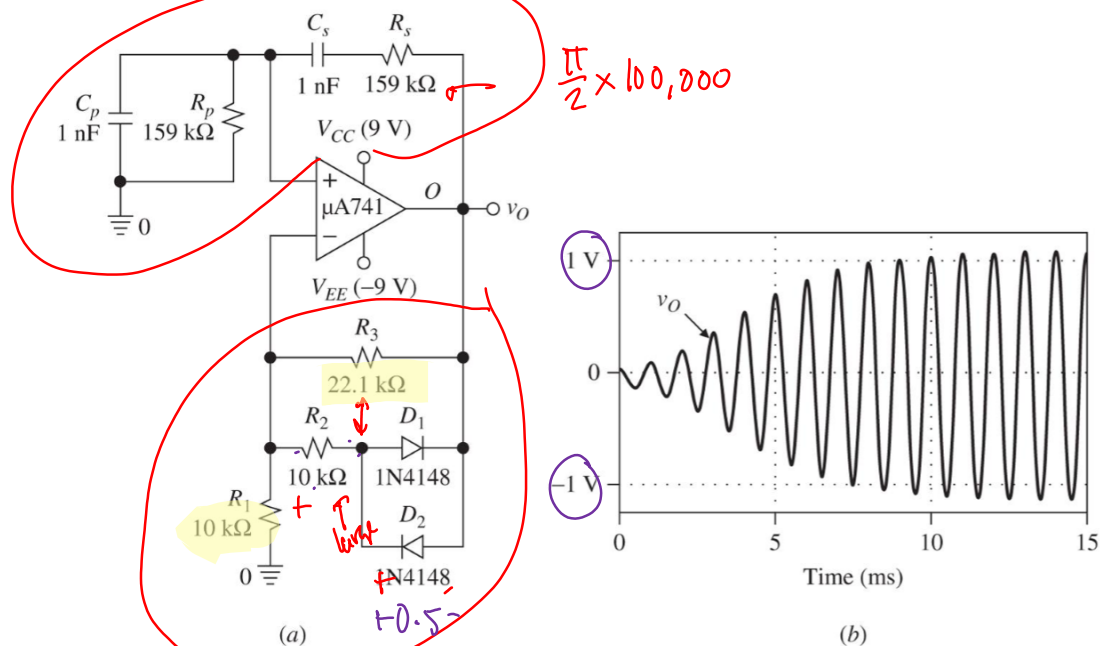Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.






Sine Wave Generators

- Oscillation accuracy and stability
 - Affected by quality of passive components and op amp dynamics
- Good choices for elements in the positive feedback network
 - Polycarbonate capacitors and thin-film resistors
- Use trimmers for exact adjustment of f_0


⑥ Amplitude control





Sine Wave Generators

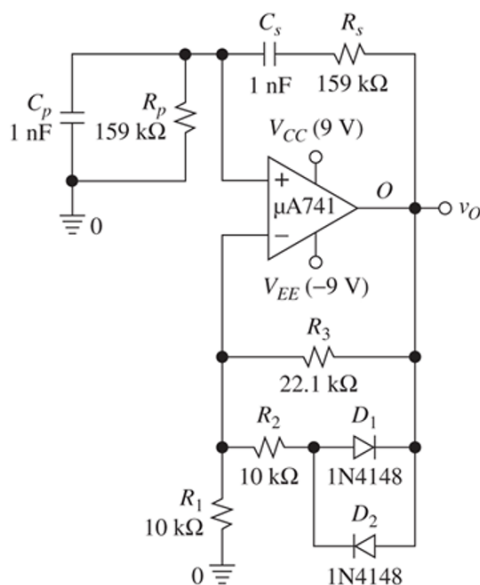

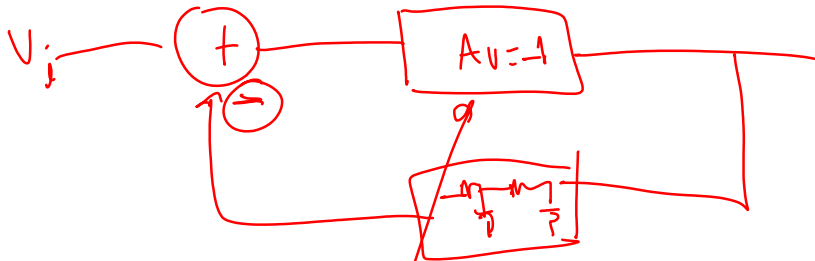- FET-input op amps used to minimize bias-current errors
- Quadrature oscillators
 - Can make an oscillator out of any second-order filter
 - Dual-integrator-loop type filters are good candidates
 - Provide two oscillations with relative phase shift of 90 degrees





Phase Shift Oscillator

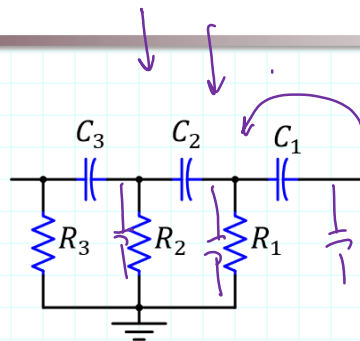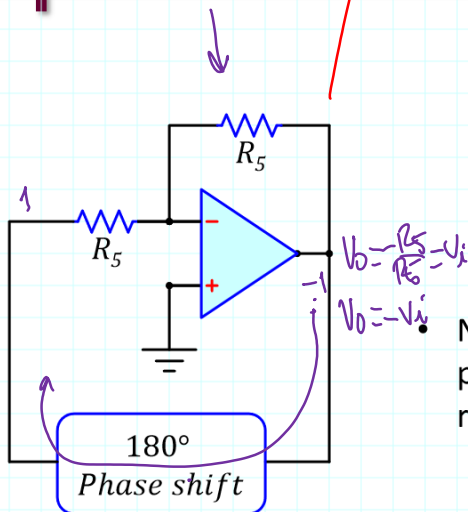



Notice that each RC stage loads the previous one, this effect can be reduced by choosing:

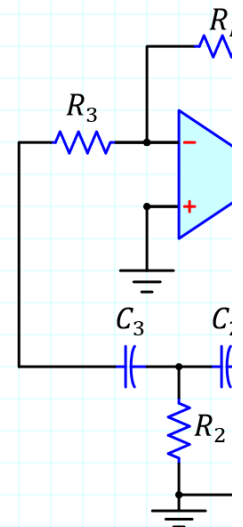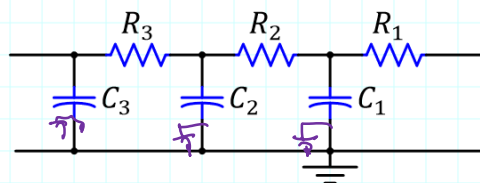- $R_3 = 10R_2 = 100R_1$, and
- $C_1 = 10C_2 = 100C_3$





Crystal Oscillator


Watch crystal

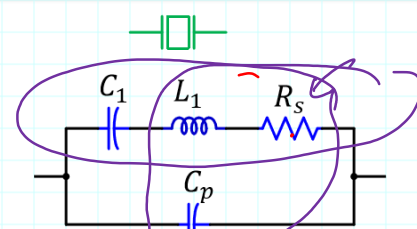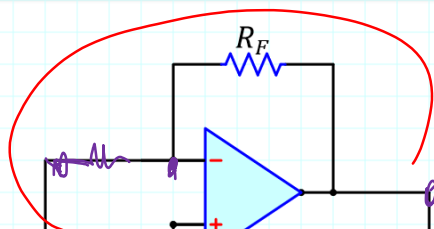



Series R
Parallel

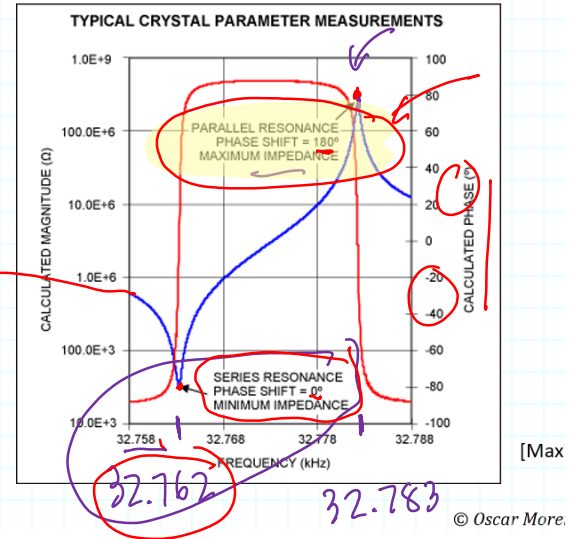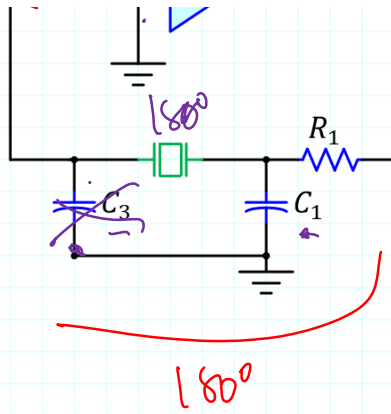

Crystal Oscillator

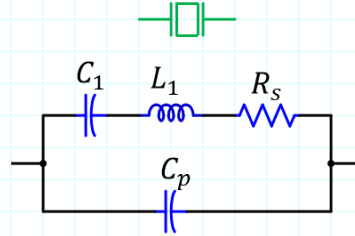

Series Resonance
Parallel Resonance

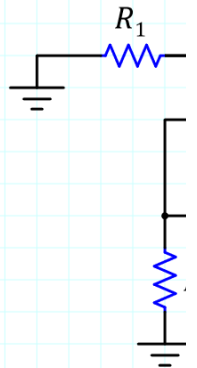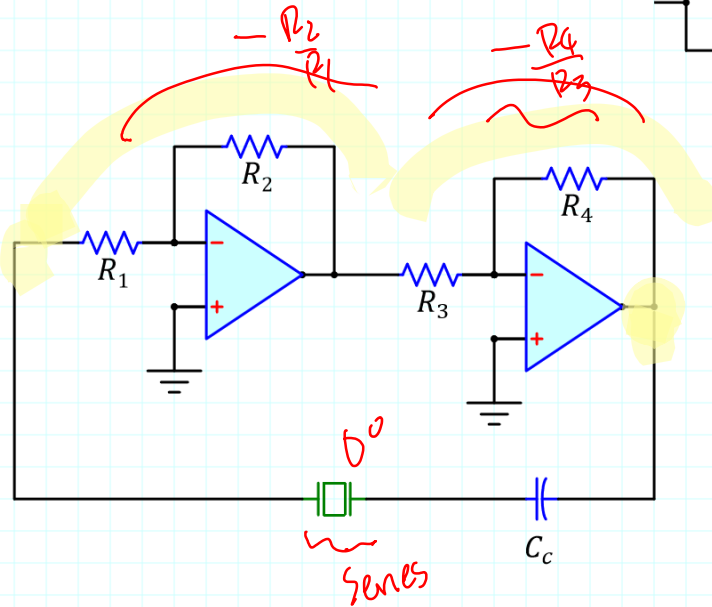

© Oscar Moreira

