

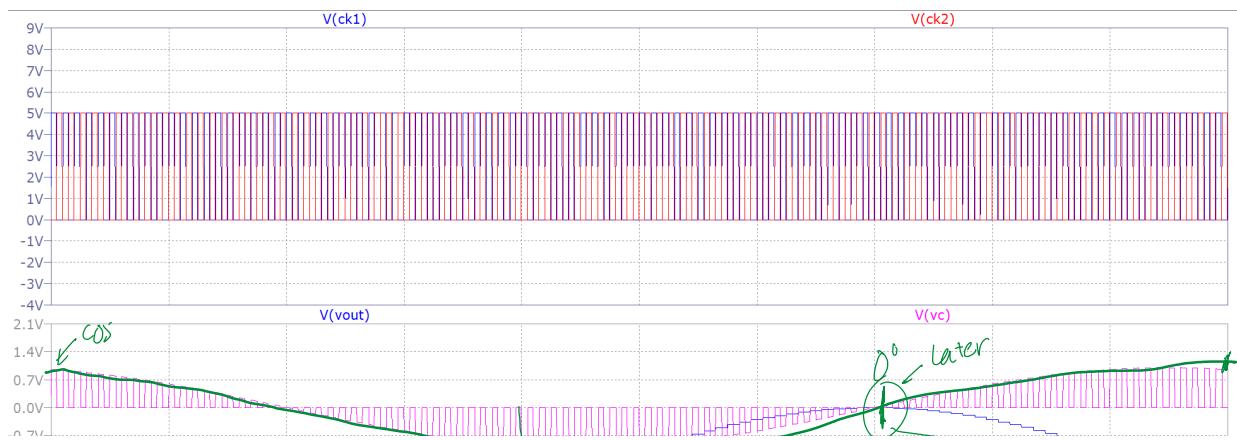


Lecture 17 - Signal Generators


Monday, October 23, 2023 6:45 PM

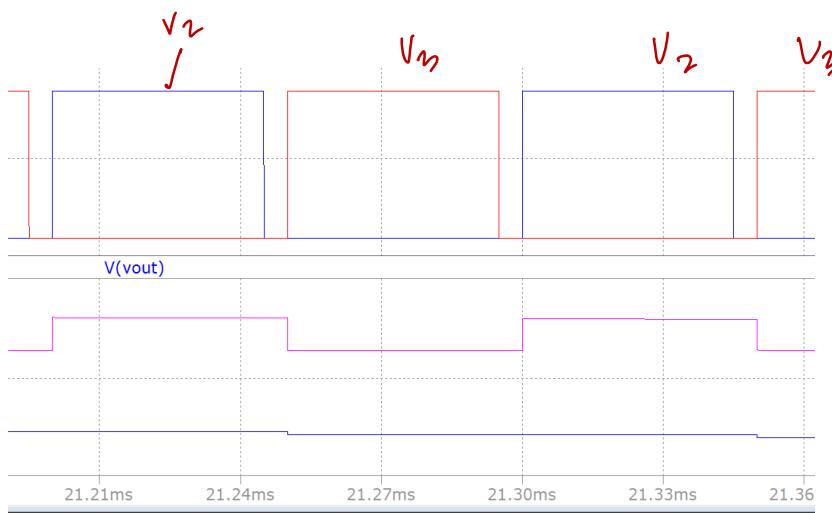

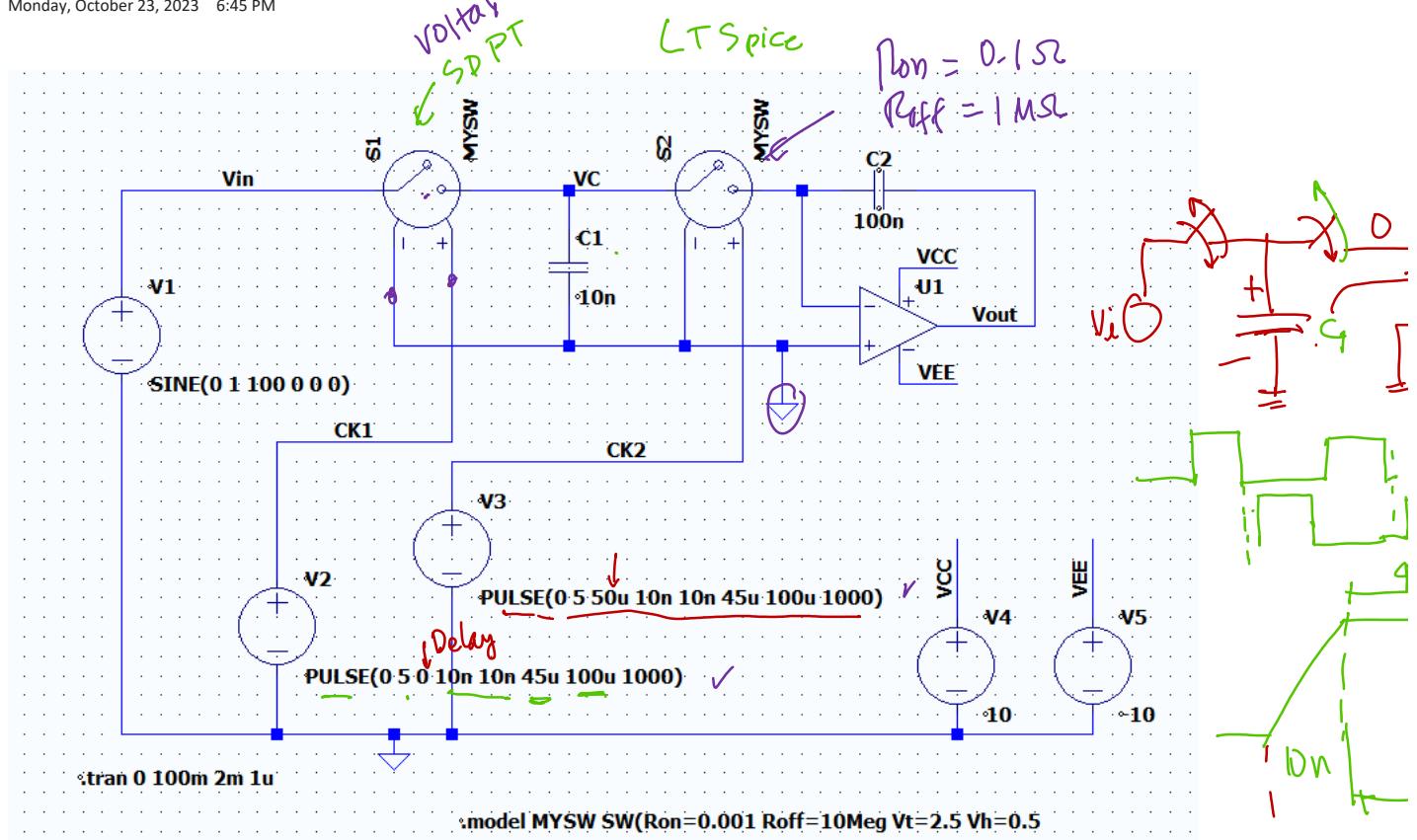



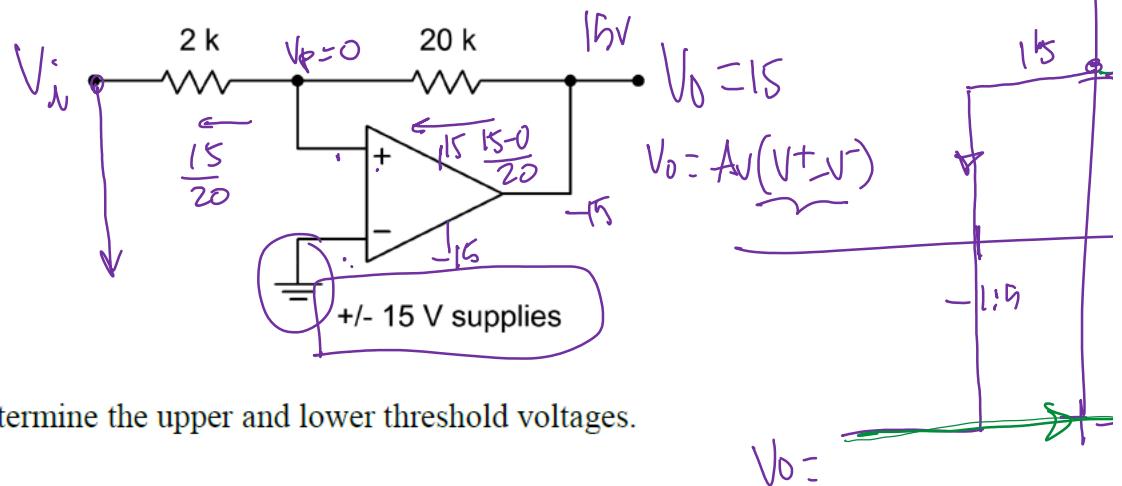
Example 7.7

Sketch the output waveform for the circuit of Figure 7.49 if the input signal is a 5 V peak sine wave.





First, determine the upper and lower threshold voltages.

$$V_i = -\frac{15}{20} 2k = -1.5$$

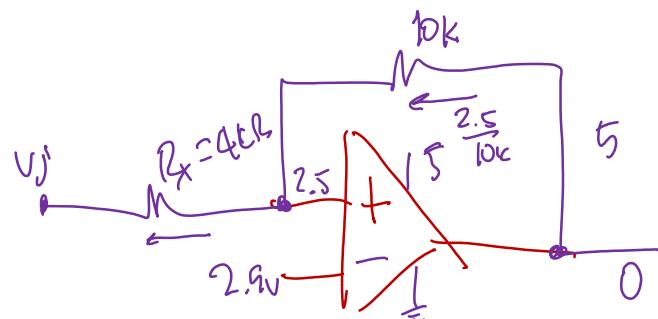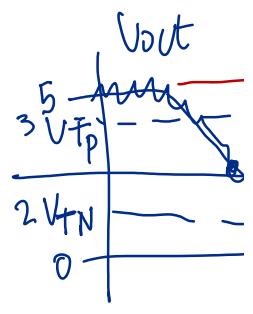
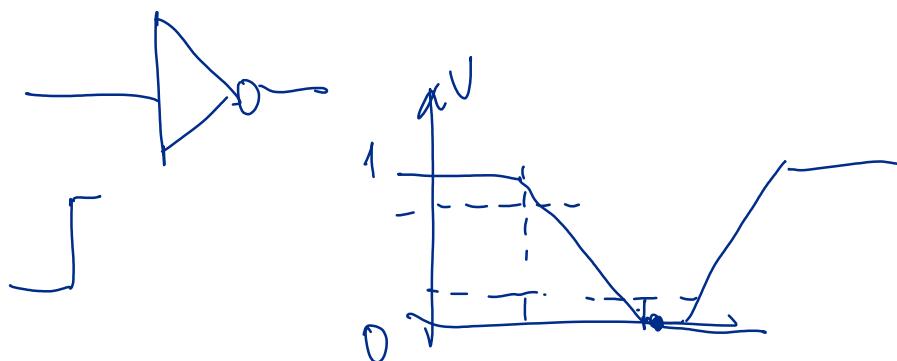


$$1.5 = \frac{2.5 - 1.5}{R_X} = \frac{2.5}{10k}$$
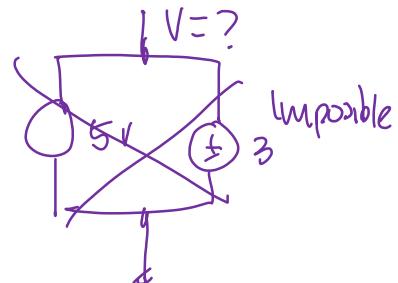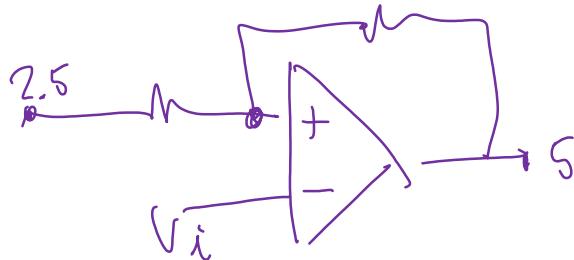
$$R_X = \frac{2.5 - 1.5}{\underline{2.5/10k}} = \frac{1 \cdot 10}{2.5} = 4k\Omega$$



Window Comparator

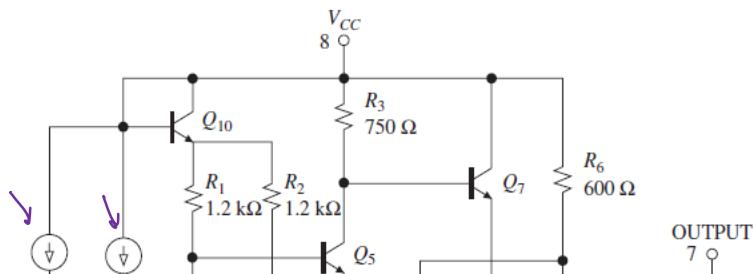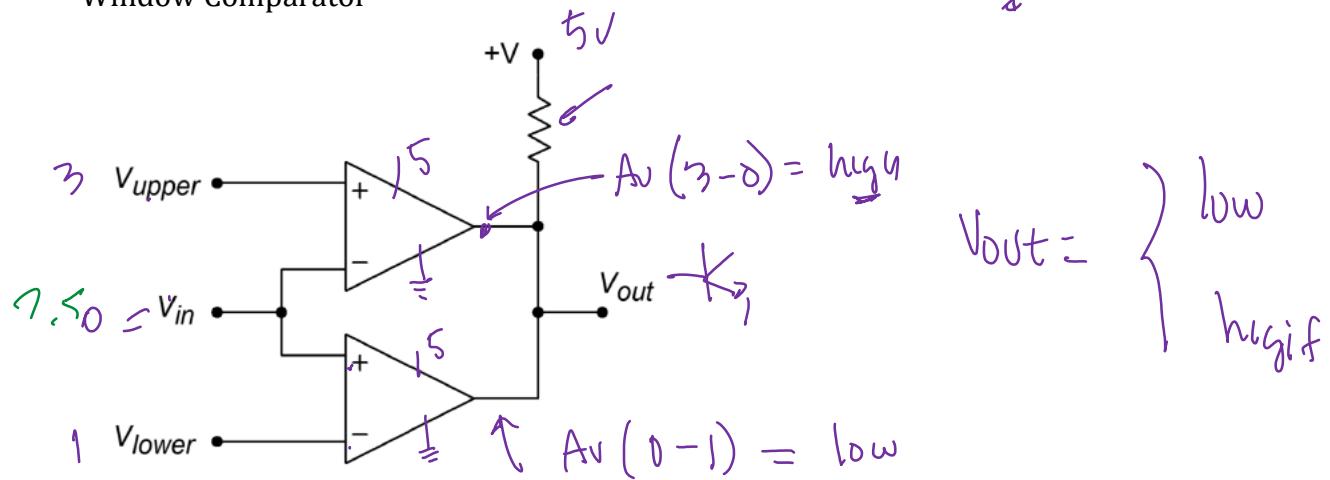

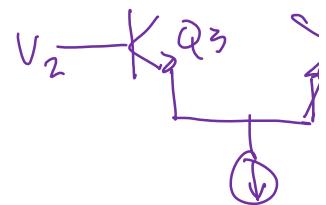
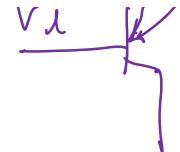
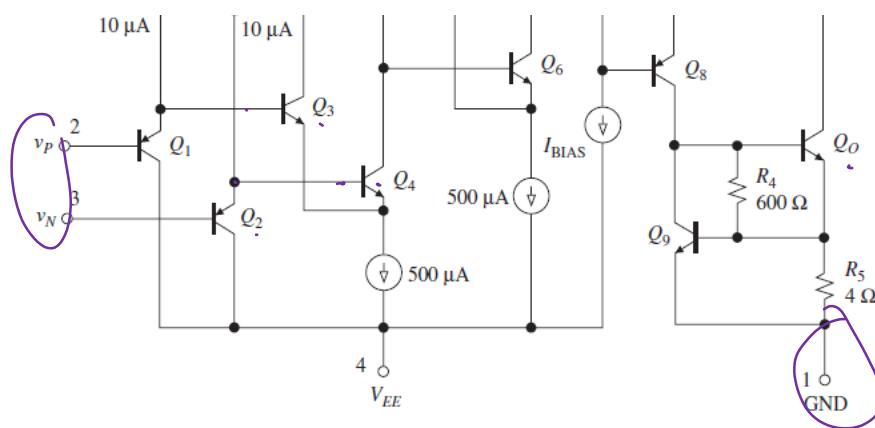


FIGURE 9.4
Simplified circuit diagram of the LM311 voltage comparator. (Courtesy of Texas Instruments.)


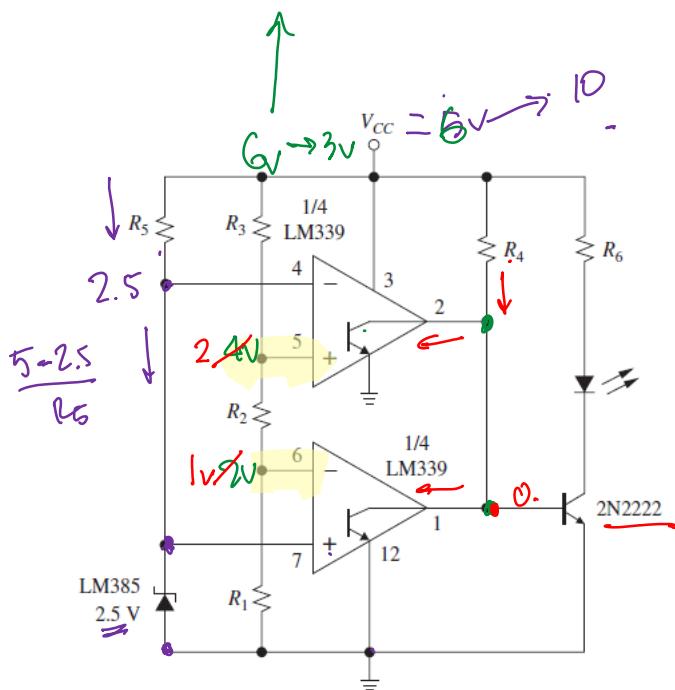



FIGURE 9.15
Power-supply monitor; LED glows as long as V_{CC} is within specification.

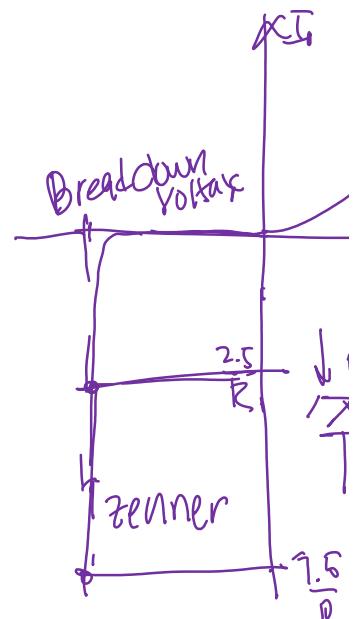

$$R_3 = R_2 = R_1$$



Single Amplifier Implementation

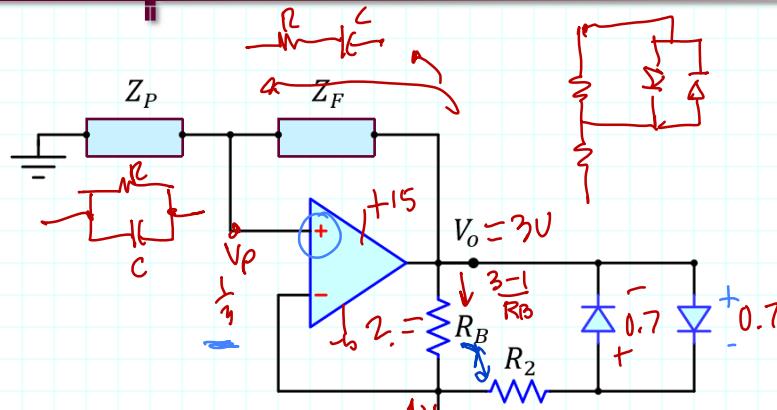

$$1 + \frac{R_B}{R_A} = 3.1$$

$$\frac{R_B}{R_A} = 2$$

$$H(s) = K_N \frac{\frac{\omega_0}{Q}s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} = V_p$$

$$R_A = 1k$$

$$1 + \frac{R_B}{2k}$$

$$\frac{2V}{2.1} \frac{1}{2k} \frac{1}{0.7}$$

$$R = \frac{1.3}{1 - \frac{2}{2.1}} = \frac{1.3(2.1)}{0.1} = \frac{2.73}{0.1} = 27.3k\Omega$$

- At low-signal levels the diodes are 0
→ The loop gain is unaffected: $T > 1$
→ Oscillation builds up

- When the oscillation grows, the diodes bring into conduction in alternating

$$\rightarrow R_2 = 2R + \varepsilon || 10R \rightarrow T < 1$$

→ Oscillation is damped by negative feedback

Oscillation will automatically stabilize

Oscillation amplitude will be dependent on diode's threshold voltage!



© Oscar Moreira


$$\frac{R \parallel \frac{1}{sC}}{R \parallel \frac{1}{sC} + R + \frac{1}{sC}} V_p = \frac{\frac{1}{1+sRC}}{\frac{R}{1+sRC} + R + \frac{1}{sC}} = \frac{\frac{1}{1+sRC}}{\frac{R+sC}{1+sRC} + R} = \frac{1}{\frac{R+sC}{1+sRC} + R}$$



Wien-Bridge Oscillator

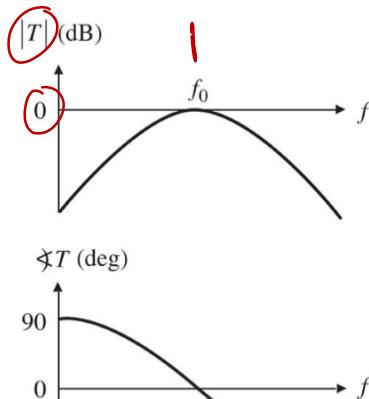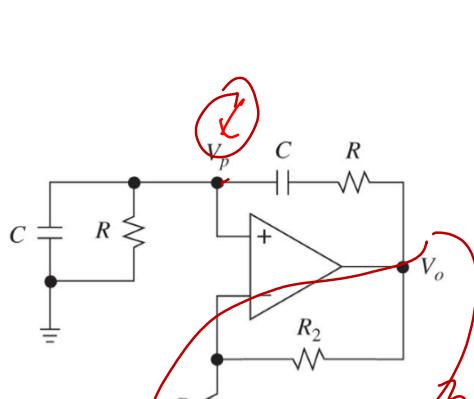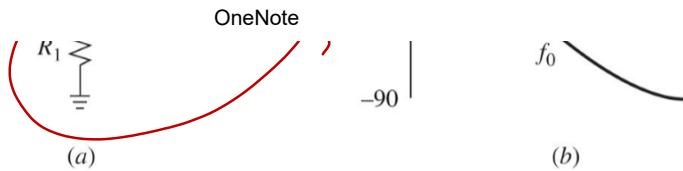Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.

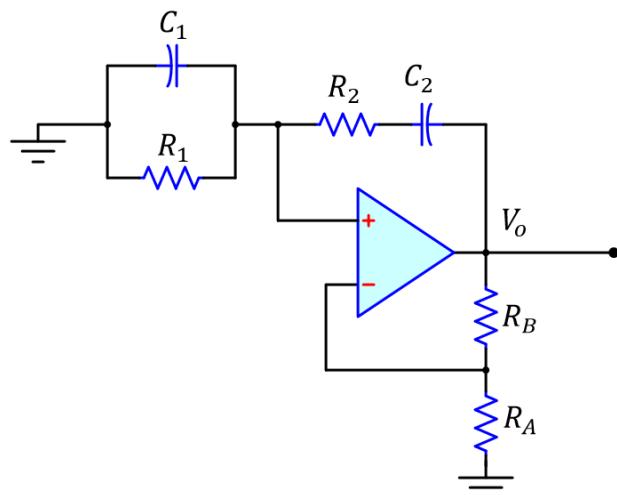


Figure 10.2 Wien-bridge circuit and its loop gain $T(jf)$ for the case $R_2/R_1=2$

© Oscar More.



Wien-Bridge Oscillator




- Wien-bridge circuit 2 uses both negative feedback
 - Circuit behavior is strongly affected by the loop gain $T(j\omega_0)$
 - If $T(j\omega_0 < 1)$, negative feedback and a stable system results
 - If $T(j\omega_0 > 1)$, positive feedback creates an unstable system, called an oscillator
 - If $T(j\omega_0 = 1)$, the system is marginally stable

© Oscar More.




Wien-Bridge Oscillator

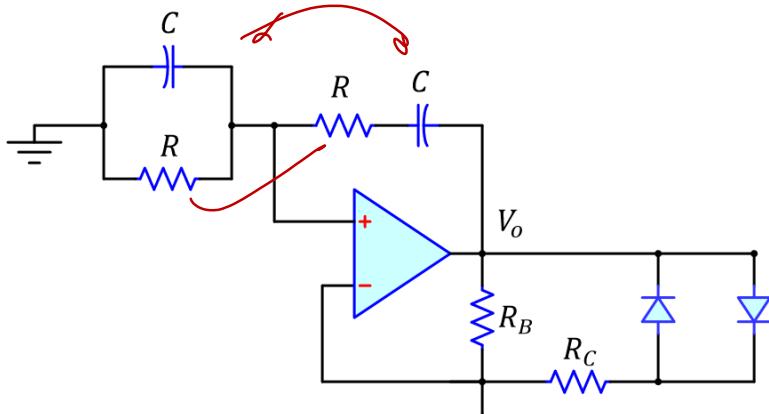For $T(j\omega_0 > 1)$,

$$A = \frac{V_o}{V_p} = 1 + \frac{R_B}{R_A}$$

$$V_p = \frac{Z_p}{Z_p + Z_s} V_o = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + \frac{1}{j\omega R}} = \frac{R}{1 + sRC}$$
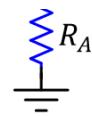
$$B(j\omega) = \frac{V_p}{V_o} = \frac{s/\omega_o}{s^2 + 3\frac{s}{\omega_o} + \frac{\omega_o^2}{R_n}}$$



$$T(j\omega) = \frac{1 + \frac{j\omega}{R_A}}{s^2 + 3\frac{s}{\omega_0} + \omega_0^2}$$


At resonant frequency $|T(j\omega_0)|$

Therefore, for sustained oscillations, $\frac{R_B}{R_A} > 2$

© Oscar More.



Wien-Bridge Oscillator

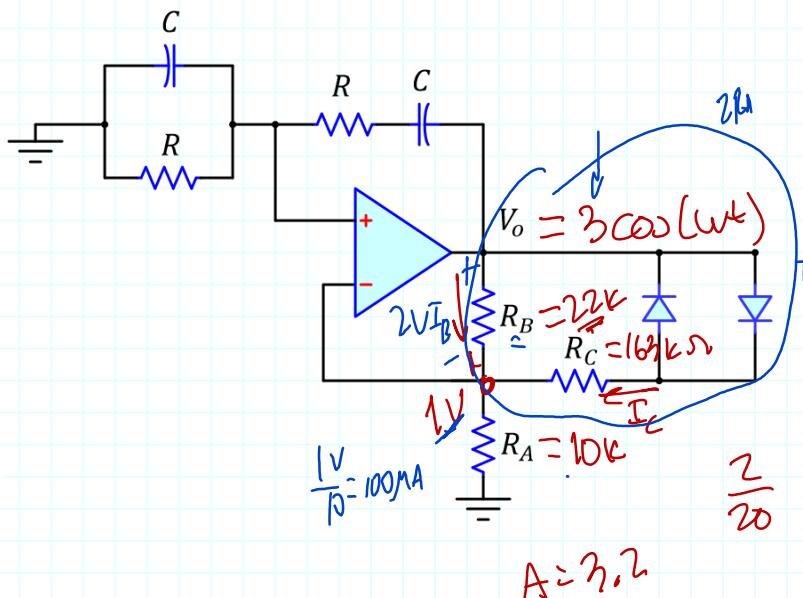


Design an oscillator such that it produces $V_o = 3 \cos(\omega t)$, and $\omega = 1 \text{ KHz}$

- For sustained oscillations, $\frac{R_B}{R_A} > 2$
- Example:
- Let $R_B = 22k\Omega$ and $R_A = 10k\Omega$, ($\frac{R_B}{R_A} = 2.2$)
- At the peak value we want to reduce the current therefore:
- $I_B = \frac{2V}{22k\Omega}$, must fall to $I_B = \frac{2V}{20k\Omega}$ so a circuit is added
- $I_C = \frac{2V}{22k\Omega} - \frac{2V}{20k\Omega} = 9.09\mu\text{A}$
- Use diode equation with $I_0 = 1 \times 10^{-12}\text{A}$
- $I_D = I_0 e^{\frac{V_D}{V_T}} \Rightarrow V_D = V_T \ln\left(\frac{9.09\mu\text{A}}{I_0}\right)$
- $R_C = \frac{2 - 0.515}{9.091\mu\text{A}} = 163k\Omega$

© Oscar More.

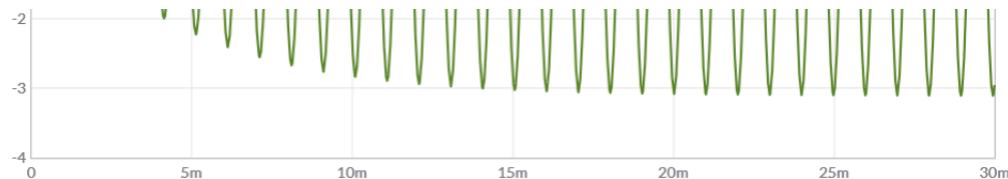
Make sure V_T is determined according to the simulation temperature






Wien-Bridge Oscillator

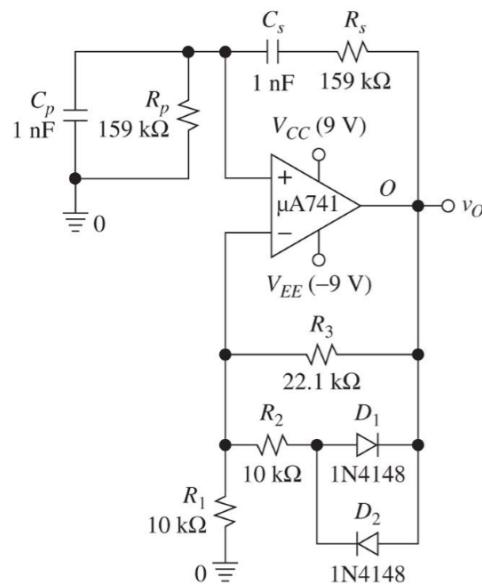Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



(a)

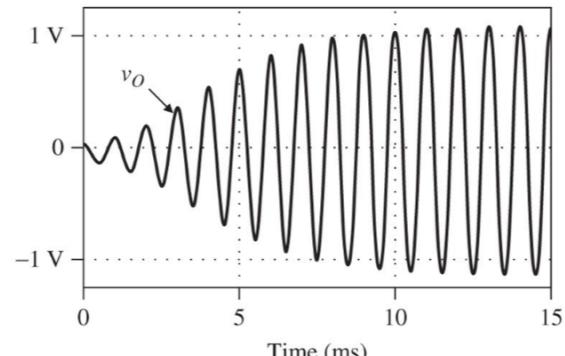

(b)

© Oscar Moreira




Sine Wave Generators

- Oscillation accuracy and stability
 - Affected by quality of passive components and op amp dynamics
- Good choices for elements in the positive feedback network
 - Polycarbonate capacitors and thin-film resistors
- Use trimmers for exact adjustment of f_0





Sine Wave Generators

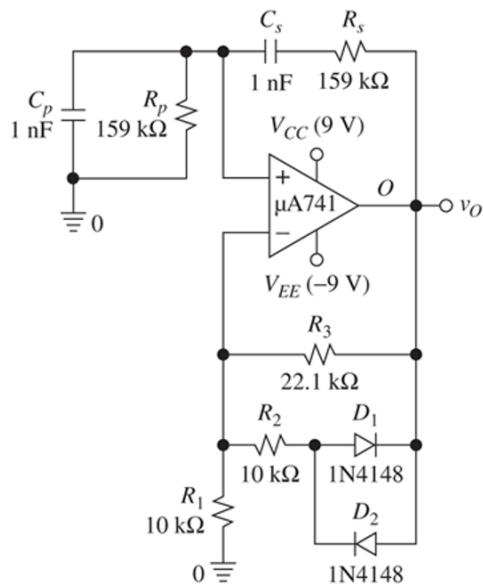


- FET-input op amps used to minimize bias-current errors
- Quadrature oscillators
 - Can make an oscillator out of any second-order filter
 - Dual-integrator-loop type filters are good candidates
 - Provide two oscillations with relative phase shift of 90 degrees




Phase Shift Oscillator

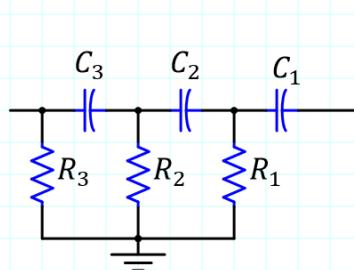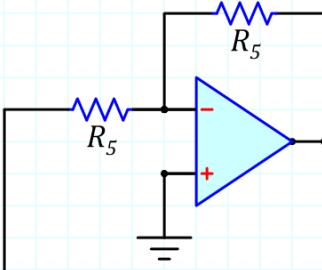


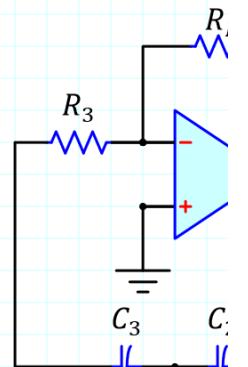
- Notice that each RC stage loads the previous one. This effect can be



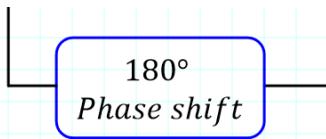

reduced by choosing:

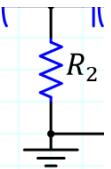
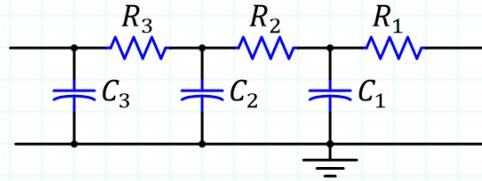
- $R_3 = 10R_2 = 100R_1$, and
- $C_1 = 10C_2 = 100C_3$




© Oscar More.



Crystal Oscillator

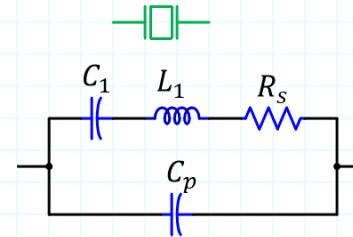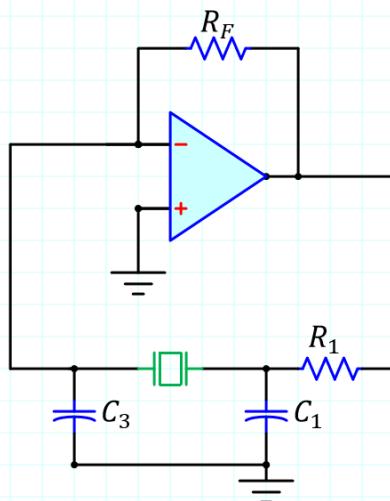

Series R
Parallel


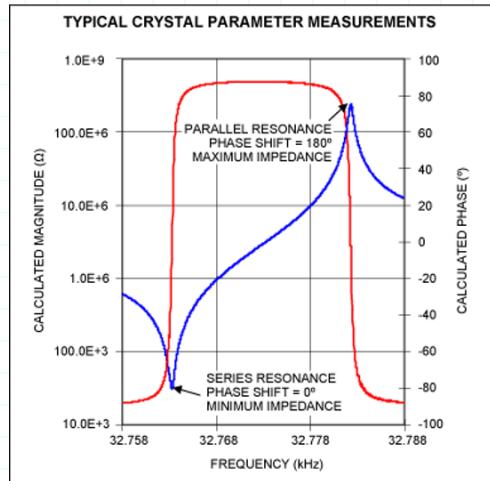


[Max]



© Oscar More.




Crystal Oscillator

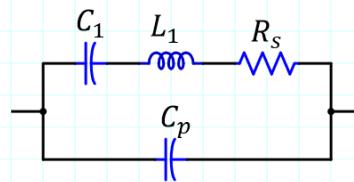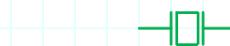

Series Resonance
Parallel Resonance

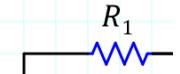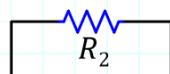

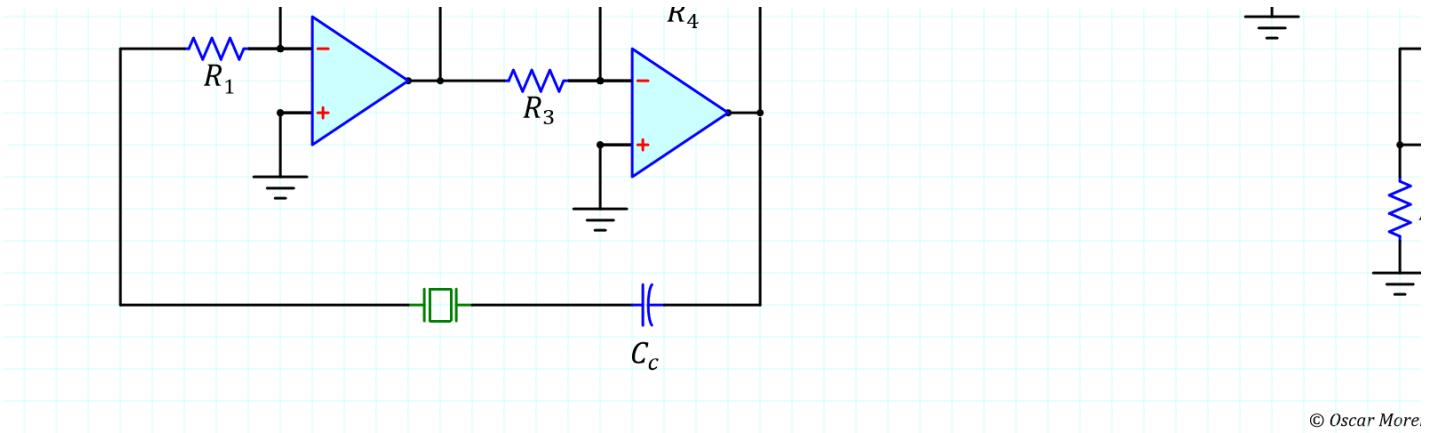

10.2 Multivibrators

- Regenerative circuits for timing applications
 - Can be bistable, astable, or monostable
- Bistable multivibrator
 - Both states are stable
 - External commands needed to force circuit to a given state

© Oscar More.



Multivibrators

- Astable multivibrator
 - Toggles spontaneously between one state and the other
- Monostable multivibrator
 - Also called one-shot


- Is stable in only one of its two states
- If forced into other state by a trigger, it returns to its stable state

© Oscar More.


46



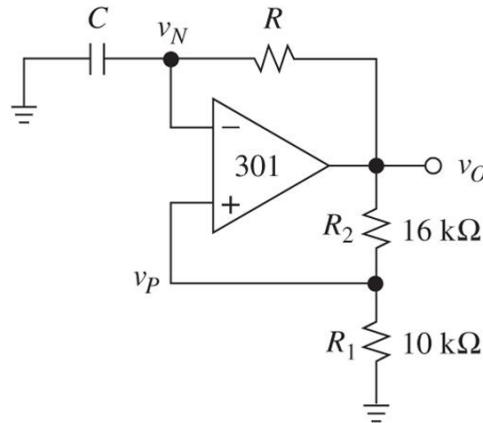Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



(a)

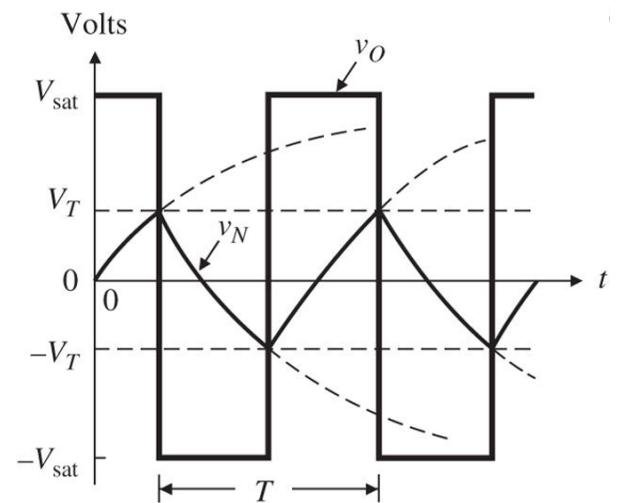

(b)

Figure 10.7 Basic free-running multivibrator

© Oscar More.



Multivibrators

- Free-running multivibrator using CMOS gates
 - CMOS logic gates are attractive when digital and analog functions run on a chip
- CMOS crystal oscillators

CMOS CRYSTAL OSCILLATORS

- Used for precise timekeeping applications
- Monostable multivibrator
- Produces a pulse of specified duration in response to a trigger

© Oscar More.



Multivibrators

Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.

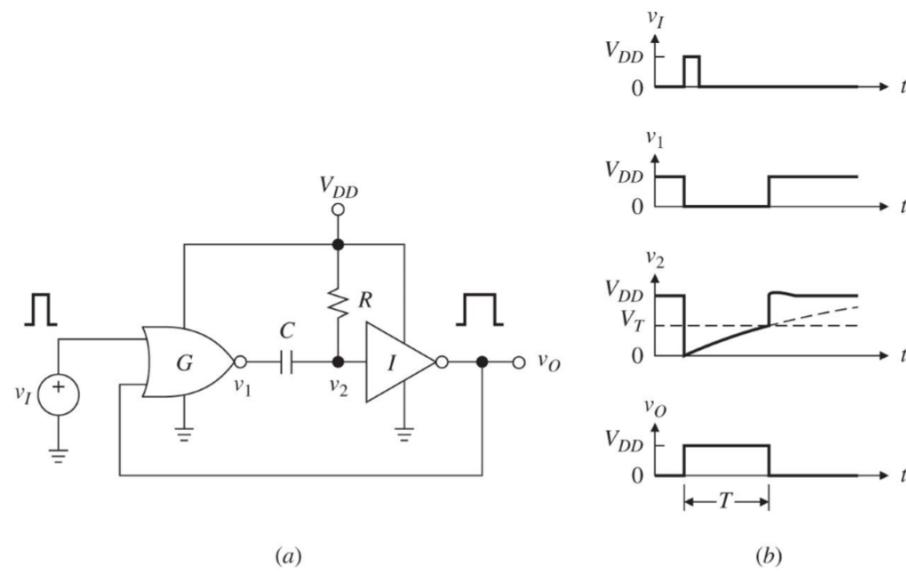


Figure 10.14 CMOS-gate one-shot

© Oscar More.



10.3 Monolithic Timers

- The 555 timer components
 - Three identical resistors
 - Two voltage comparators

- A flip-flop
- A BJT switch
- The 555 timer is available in bipolar and CMOS versions
 - CMOS version has low power consumption and very high input im

© Oscar More.



Monolithic Timers

- The 555 timer can be configured for astable or monostable operation
- The 555 timing characteristics
 - Can be modified via the CONTROL input
 - Pulse-position modulation: in astable operation
 - Pulse-width modulation: in monostable operation
 - Timer/counter circuits are used for applications with long delays

© Oscar More.



10.4 Triangular Wave Generators


- Triangular waves generated by alternately charging and discharging capacitor with a constant current
- Slope control

- Charge and discharge times can be adjusted independently to generate asymmetric waves

© Oscar Moreira



Basic Triangular/Square Wave Generator

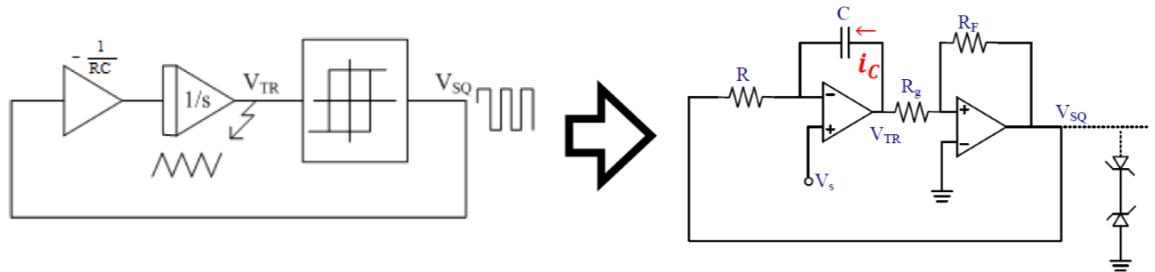

Non-inverting Schmitt trigger toggles between V_{OH} and V_{OL}
The transition occurs when:


$$V_{TR}(t) = V_{TL/H} = -\left(\frac{R_G}{R_F}\right)V_{OH/L}$$

Because of negative feedback, the current through the capacitor is given by:

$$i_C(t) = \frac{V_s - V_{SQ}(t)}{R}$$

Between transitions V_{SQ} can be considered a DC voltage, so V_{TR} is linearly increasing or decreasing with a constant current.
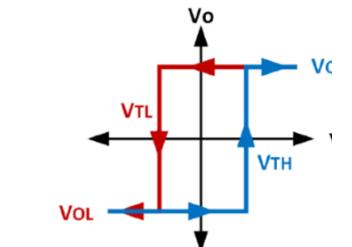
$$\pm\Delta V_{TR}(t)_{t_0 \rightarrow t_1} = \left(\frac{i_C}{C}\right)\Delta t = \left(\frac{V_s - V_{OL/H}}{RC}\right)\Delta t$$



if $V_{SQ} = V_{OL}$ $V_{TR} \uparrow$
if $V_{SQ} = V_{OH}$ $V_{TR} \downarrow$

Inversion from V_{TR} to V_{SQ} !

© Oscar Moreira



Basic Triangular/Square Wave Generator

V_{TR} will toggle between two voltages: $\Delta V_{TR} = V_{TH} - V_{TL} = \left(\frac{R_G}{R_F}\right)(V_{OH} - V_{OL})$

The rise/fall times of the triangular waveform are given by: $\Delta t_{R/F} = \frac{\pm\Delta V_{TR}}{\left(\frac{\delta V_{TR}}{\delta t}\right)} = RC \left(\frac{R_G}{R_F}\right) \frac{\pm(V_{OH} - V_{OL})}{(V_s - V_{OL/H})}$

Assuming symmetrical saturation voltages:


$V_{TH} = V_{TL}$

Assuming Symmetrical Saturation Voltages.

$$(V_{OH} = -V_{OL} = V_{SAT})$$

$$\Delta t_{R/F} = 2RC \left(\frac{R_G}{R_F} \right) \frac{V_{SAT}}{(V_{SAT} \pm V_S)}$$
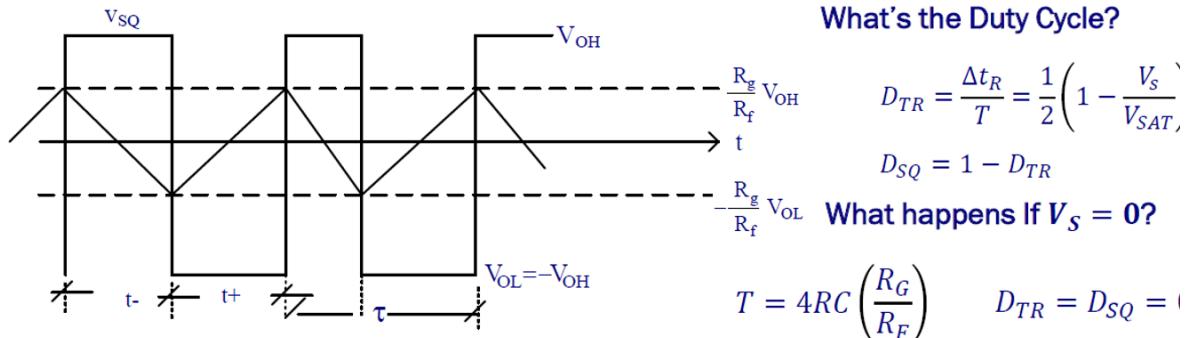
$$\text{The oscillation period is: } T = \Delta t_R + \Delta t_F = 4RC \left(\frac{R_G}{R_F} \right) \frac{V_{SAT}^2}{(V_{SAT}^2 - V_S^2)}$$




© Oscar More.

54



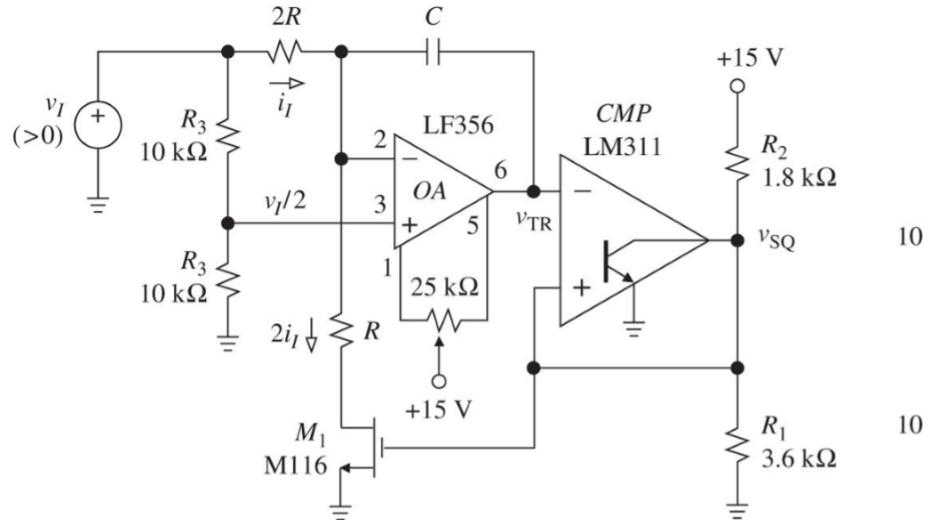Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



(a)

© Oscar More.



10.5 Sawtooth Wave Generators

- Sawtooth cycle generated by charging a capacitor at a constant rate and then rapidly discharging it using a switch

- Circuit can function as current-controlled oscillator (CCO)
- Common application: electronic music



© Oscar More.

56



Voltage-controlled triangular/square-wave oscillator

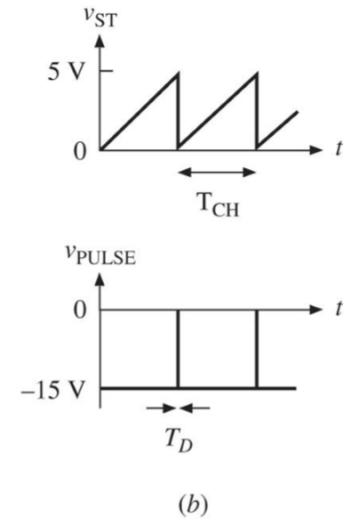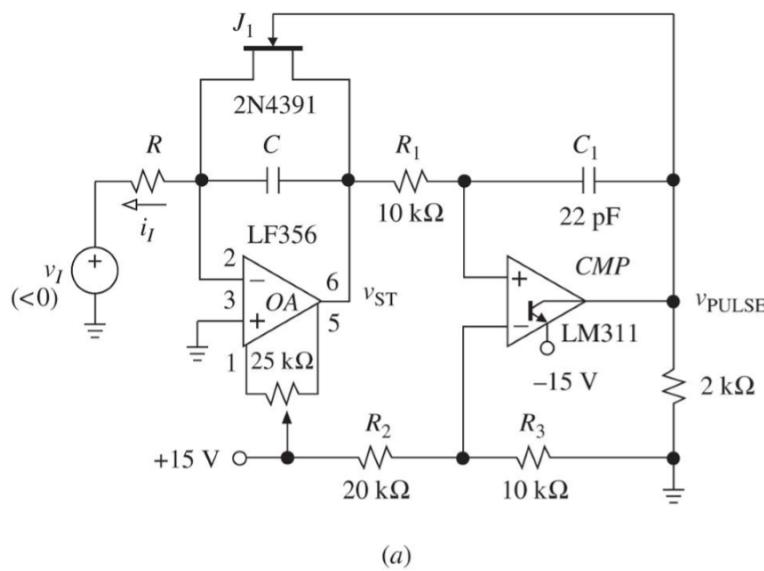Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



© Oscar More.



10.6 Monolithic Waveform Generators

- Circuits are designed to provide basic waveforms with the minimum number of external components

- Also called function generators
- Waveform generator contains a VCO that generates the triangle and square waves
 - Sine wave generated from triangular wave by on-chip wave shaper

© Oscar More.



Monolithic Waveform Generators

- Grounded-capacitor VCOs
 - Charge and discharge a grounded capacitor
 - Rates controlled by programmable current generators
 - Popular products: NE566 function generator and ICL 8038 waveform converter
- Emitter-coupled VCOs
 - Popular products: XR2206/07 monolithic function generator and A/D converter

© Oscar More.




Monolithic Waveform Generators

Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.

$$\underline{V_{CC}}$$

$$\underline{v_{TR}}$$

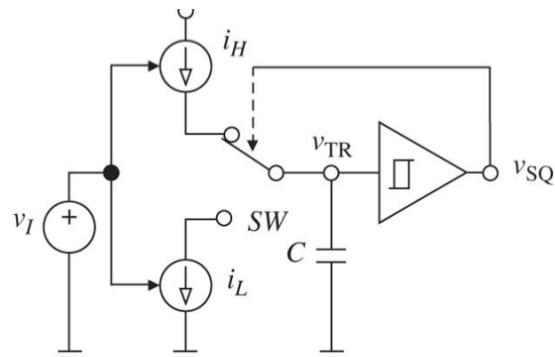

(a)

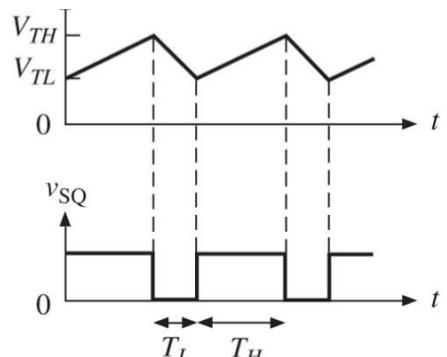



Figure 10.25 Grounded-capacitor VCO

© Oscar Morel



Monolithic Waveform Generators

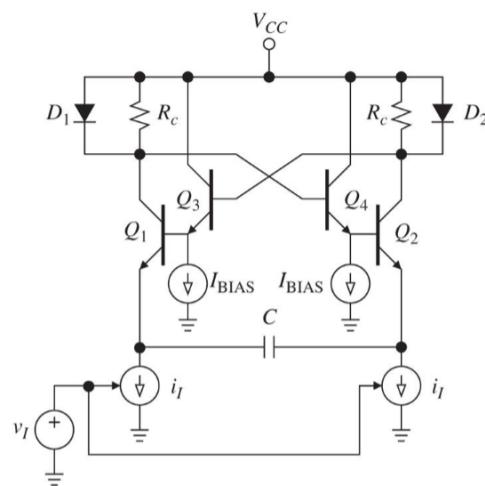Copyright © McGraw-Hill Education. All rights reserved. No reproduction or distribution without the prior written consent of McGraw-Hill Education.



(a)

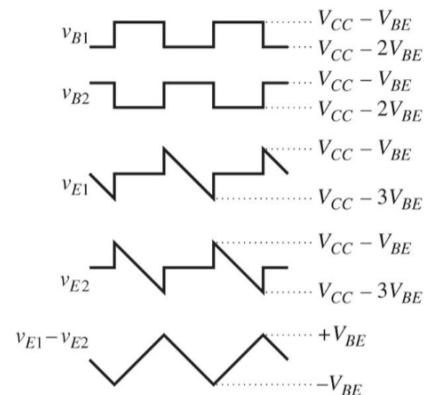


Figure 10.30 Emitter-coupled VCO

© Oscar Morel



10.7 V-F and F-V Converters

- ## ➤ Voltage-to-frequency converter (VFC)

- Accepts analog input
- Generates a pulse train with frequency

$$f_O = kv_I \quad (10.27)$$

where k is the VFC sensitivity in hertz per volt

- **Performance specifications of VFCs**
 - Wide dynamic range
 - High frequency operation

© Oscar More.



V-F and F-V Converters

- Performance specifications of VFCs (cont'd.)
 - Low linearity error
 - High scale-factor accuracy and stability with temperature and supply
- VFC categories
 - Wide-sweep multivibrators
 - Charge-balancing VFCs

© Oscar More.



V-F and F-V Converters

- Frequency-to-voltage converter (FVC)

➤ Accepts a periodic waveform of frequency f_I

➤ Yields analog output voltage

$$v_O = k f_I$$

where k is the FVC sensitivity in volts per hertz

➤ Application: tachometers